



## AUTUMN MID SEMESTER EXAMINATION-2023

School of Computer Engineering  
Kalinga Institute of Industrial Technology, Deemed to be University  
Digital System Design  
[EC 20005]

Time: 1 1/2 Hours

Full Mark: 40

*Answer any four Questions including Question No. 1 which is compulsory.  
The figures in the margin indicate full marks. Candidates are required to give their answers in their own words as far as practicable and all parts of a question should be answered at one place only.*

1. Answer all the questions. [ 2 x 5 ]
  - a) Write some advantages of using digital systems over analog systems? What are the three major design specifications for an IC chip?
  - b) Perform the following operation using signed 2's complement method: -6-(-13).
  - c) Design a full subtractor circuit using two half subtractors.
  - d) Differentiate between bit-wise and logical operators with examples.
  - e) Simplify the Boolean function  $f = AB + (A+B).(A+B)$
2.
  - a) What is Moore's prediction? Explain the major stages of VLSI design flow with relevant block diagram.
  - b) What are the different types of modelling techniques in Verilog? Explain any two of them using suitable example.[ 5+5 Marks ]
3.
  - a) Obtain the minimized expression for the following 4 variable Boolean expression using K-map method and implement the minimized expression using NOR gates only.
$$F(A,B,C,D) = \sum m(11,12,14) + d(3,4,6)$$
  - b) Prove the following using Boolean algebra:  $(A+B).(\overline{A}+C).(B+C) = (A+B).(\overline{A}+C)$[ 5+5 Marks ]
4.
  - a) Convert gray code 11011 to binary. Design a 4-bit gray to binary code converter with proper steps.
  - b) Write HDL code for the 4-bit gray to binary converter in gate-level modelling technique with test bench code.[ 5+5 Marks ]
5.
  - a) What is the difference between encoder and decoder? Write the HDL code for a 3:8 decoder in data-flow modelling technique with test bench code.
  - b) Implement the following boolean function using 3:8 active low decoder circuit:

$$F(A,B,C,D) = \sum m(1,3,4,5,7) \quad [5+5 \text{ Marks}]$$